

# SME309 Lab Report - Single Cycle Processor

By HUANG Guanchao, SID 11912309, from the School of Microelectronics. All of the materials, including source code, diagrams and the report itself can be retrieved at [my GitHub repo](#).

- Code edited in [VSCode](#), with support from extensions [TerosHDL](#) and [FPGA Develop Support](#).
- Compiled and simulated with Vivado 2021.1, ModelSim 2020.1
- Testbench assembled using Keil uVision 5

## SME309 Lab Report - Single Cycle Processor

Instruction Set Architecture

Processor Implementation

Program Counter

Register File

Decoder

Conditional Logic

Control Unit

ALU

Extend

Single Cycle Processor

Testbench

Testbench for Memory Operations

Testbench for Data-Path Operations

Testbench for Branch Instruction

Testbench for Flags and Condition Logic

Conclusion

## Instruction Set Architecture

The single cycle processor is implemented based on reduced 32bit ARMv3 instruction set architecture, which provides support for the following instructions:

- Datapath instructions

- **ADD**
- **SUB**
- **AND**
- **ORR**

Immediate number with rotation, register with shift, and register-shifted register are not supported for **Src2**.

- Branching instruction **B**

- Memory instructions

- **LDR**
- **STR**

Register bias, as well as preindex and postindex for accessing memory are not supported.


Instructions with conditions and flags setting are supported.

The register file is of 16 registers, with **R15** dedicated for program counter.

## Processor Implementation

The processor diagram is shown below.


This diagram is redrawn with **draw.io**

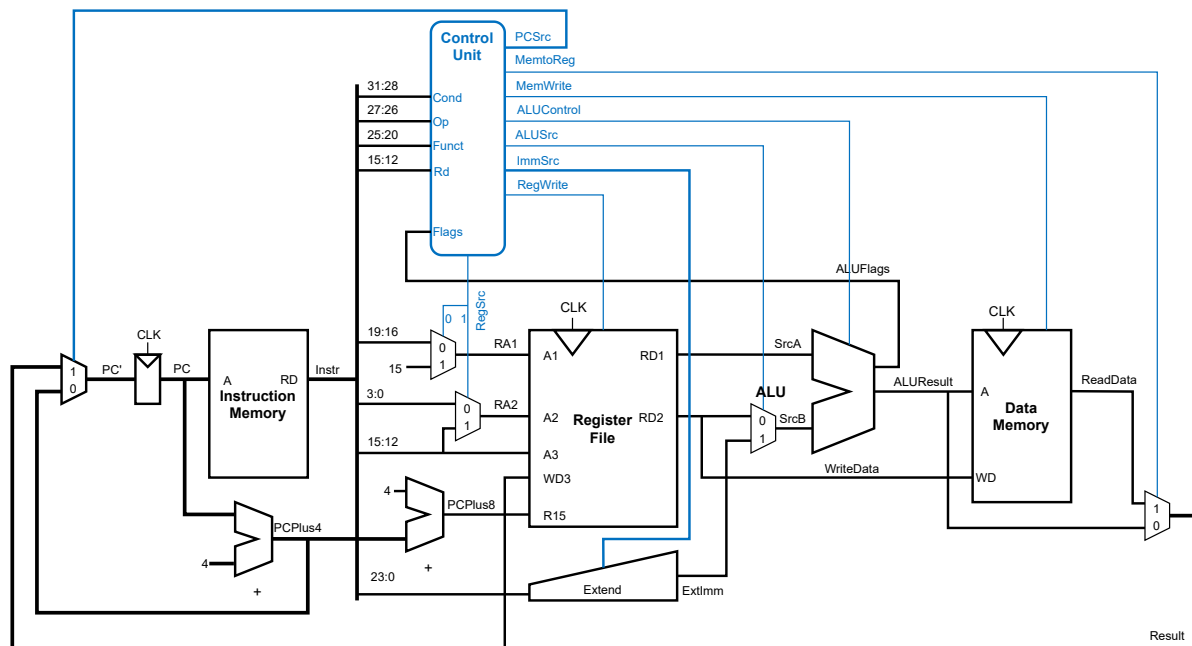

Some of the following elaborations for entities are generated with TerosHDL documentation tool.

### Program Counter

File: **ProgramCounter.v**

 

- Ports

Port name	Direction	Type
CLK	input	
Reset	input	
PCSrc	input	
Result	input	[31:0]
PC	output	[31:0]
PC_Plus_4	output	[31:0]

- Signals

Name	Type	Description
next_PC	reg [31:0]	Intermediate wire next_PC
PC_tmp	reg [31:0]	Sequential, synchronous reset, and updates current_PC

- Verilog Implementation

```


1  module ProgramCounter (
2      input CLK,
3      input Reset, // reset is high-active
4      input PCSrc, // PC source
5      input [31:0] Result, // From ALU
6
7      output [31:0] PC,
8      output [31:0] PC_Plus_4
9  );
10
11
12  //! Intermediate wire `next_PC`
13  reg [31:0] next_PC;
14  //! Combinational, defines `PC_Plus_4`
15  assign PC_Plus_4 = PC + 4;
16
17
18  //! Sequential, synchronous reset, and updates `current_PC`
19  reg [31:0] PC_tmp;
20
21  always @(posedge CLK)
22      if (Reset == 1'b1)
23          PC_tmp <= 0;
24      else
25          PC_tmp <= next_PC;
26
27  assign PC = PC_tmp;
28
29  //! Combinational, defines `next_PC`
30  always @(*)
31      if (PCSrc == 1'b0)
32          next_PC = PC_Plus_4;
33      else

```

```
34         next_PC = Result;
35
36
37     endmodule
```

Register File

File: RegisterFile.v

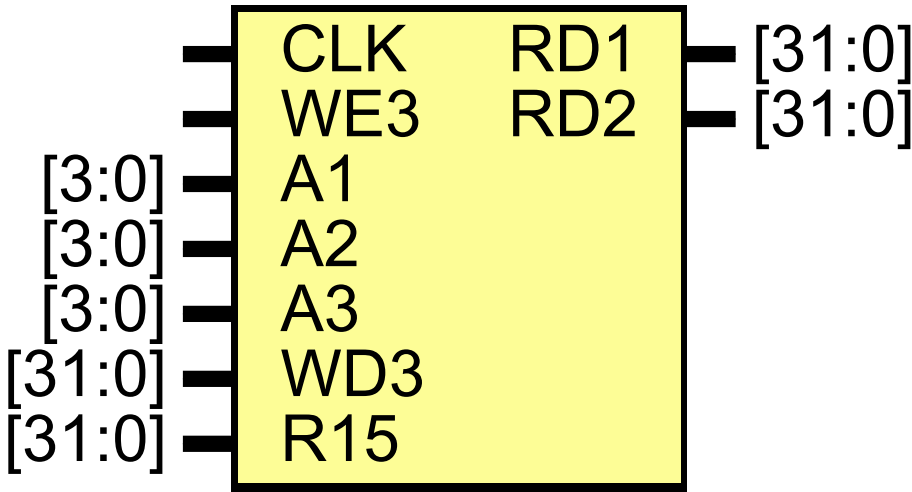

• Ports

Port name	Direction	Type
CLK	input	
WE3	input	
A1	input	[3:0]
A2	input	[3:0]
A3	input	[3:0]
WD3	input	[31:0]
R15	input	[31:0]
RD1	output	[31:0]
RD2	output	[31:0]

• Signals

Name	Type
RegBankCore	reg [31:0]

• Verilog Implementation

```
1 // RegisterFile.v
2 module RegisterFile(
```


```

3     input CLK,
4     input WE3, // high active
5     input [3:0] A1, // Read index1
6     input [3:0] A2, // Read index2
7     input [3:0] A3, // Write index
8     input [31:0] WD3, // Write data
9     input [31:0] R15, // R15 Data in
10
11     output reg [31:0] RD1, // Read data1
12     output reg [31:0] RD2 // Read data2
13 );
14
15
16     reg [31:0] RegBankCore[0:14];
17
18
19     //! Sequential, writes `WD3` into `RegBankCore` at the rising edge of clk
20     always @(posedge CLK)
21         if (WE3)
22             RegBankCore[A3] <= WD3;
23
24
25     //! Combinational, defines `RD1`
26     always @(*)
27         if (A1 == 4'b1111)
28             RD1 = R15;
29         else
30             RD1 = RegBankCore[A1];
31
32
33     //! Combinational, defines `RD2`
34     always @(*)
35         if (A2 == 4'b1111)
36             RD2 = R15;
37         else
38             RD2 = RegBankCore[A2];
39
40
41     endmodule

```

## Decoder

File: `Decoder.v`

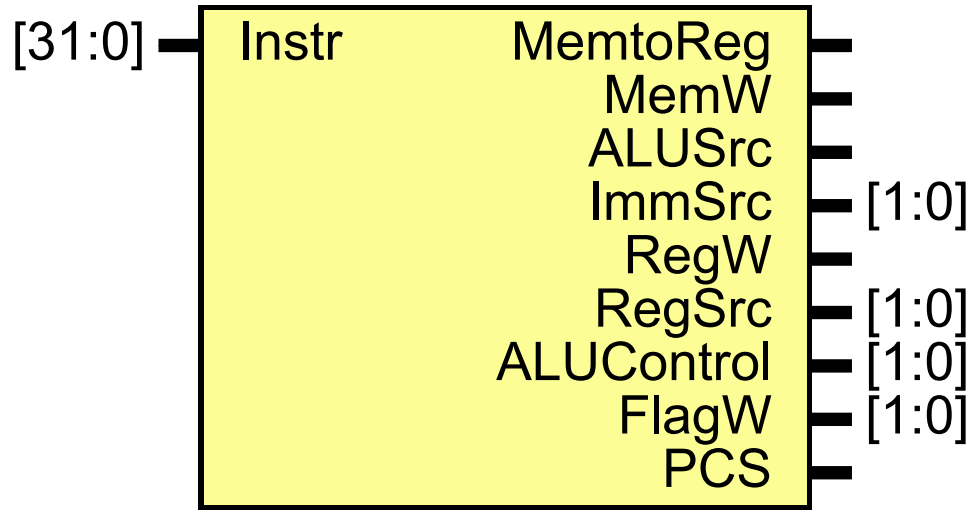

- Ports

Port name	Direction	Type
<code>Instr</code>	input	[31:0]
<code>MemtoReg</code>	output	
<code>MemW</code>	output	
<code>ALUSrc</code>	output	
<code>ImmSrc</code>	output	[1:0]
<code>RegW</code>	output	
<code>RegSrc</code>	output	[1:0]
<code>ALUControl</code>	output	[1:0]
<code>FlagW</code>	output	[1:0]
<code>PCS</code>	output	

- Signals

Name	Type
<code>ALUOp</code>	reg
<code>Branch</code>	reg
<code>Main</code>	reg [9:0]
<code>ALU</code>	reg [3:0]

- Verilog Implementation

```

1  module Decoder(
2      input [31:0] Instr,
3
4      output reg MemtoReg,
```

```


5     output reg MemW,
6     output reg ALUSrc,
7     output reg [1:0] ImmSrc,
8     output reg RegW,
9     output reg [1:0] RegSrc,
10    output reg [1:0] ALUControl,
11    output reg [1:0] FlagW,
12    output reg PCS
13 );
14
15 reg ALUOp;
16 reg Branch;
17
18 reg [9:0] Main;
19 /// Main Decoder
20 always @(*)
21 begin
22     casex ({Instr[27:25], Instr[20]}) // Op, Funct5, Funct0
23         4'b000x :
24             Main = 10'b0000xx1001; // DP reg
25         4'b001x :
26             Main = 10'b0001001x01; // DP imm
27         4'b01x0 :
28             Main = 10'b0x11010100; // STR
29         4'b01x1 :
30             Main = 10'b0101011x00; // LDR
31         default:
32             Main = 10'b1001100x10; // B
33     endcase
34     {Branch, MemtoReg, MemW, ALUSrc, ImmSrc, RegW, RegSrc, ALUOp} = Main;
35 end
36
37 reg [3:0] ALU;
38 /// ALU Decoder
39 always @(*)
40 begin
41     case ({ALUOp, Instr[24:20]}) // ALUOp, Funct4:1, Funct0
42         6'b101000 :
43             ALU = 4'b0000; // ADD
44         6'b101001 :
45             ALU = 4'b0011; // ADDS
46         6'b100100 :
47             ALU = 4'b0100; // SUB
48         6'b100101 :
49             ALU = 4'b0111; // SUBS
50         6'b100000 :
51             ALU = 4'b1000; // AND
52         6'b100001 :
53             ALU = 4'b1010; // ANDS
54         6'b111000 :
55             ALU = 4'b1100; // ORR
56         6'b111001 :
57             ALU = 4'b1110; // ORRS
58         default:
59             ALU = 4'b0000; // Not DP
60     endcase
61     {ALUControl, FlagW} = ALU;
62 end

```

```
63
64     //! PC Logic
65     always @(*)
66         PCS = Branch;
67
68     endmodule
```

Conditional Logic

File: CondLogic.v

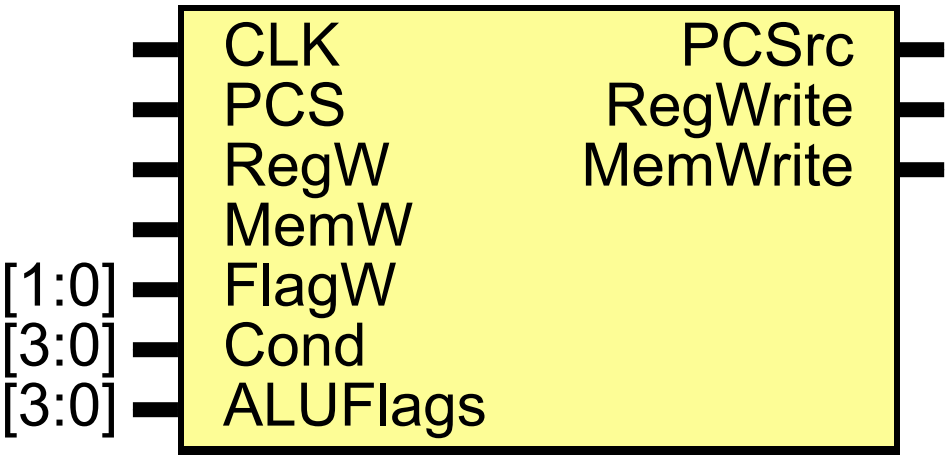

- Ports

Port name	Direction	Type
CLK	input	
PCS	input	
RegW	input	
MemW	input	
FlagW	input	[1:0]
Cond	input	[3:0]
ALUFlags	input	[3:0]
PCSrc	output	
RegWrite	output	
MemWrite	output	

- Signals



Name	Type
CondEx	reg
N	reg
Z	reg
C	reg
V	reg

- Verilog Implementation

```

1  module CondLogic(
2      input CLK,
3      input PCS,
4      input RegW,
5      input MemW,
6      input [1:0] FlagW,
7      input [3:0] Cond,
8      input [3:0] ALUFlags,
9
10     output PCSrc,
11     output RegWrite,
12     output MemWrite);
13
14     reg CondEx;
15     reg N = 0, Z = 0, C = 0, V = 0;
16     wire [1:0] FlagWrite = FlagW[1:0] & {2{CondEx}};
17
18     /// Output stage
19     assign {PCSrc, RegWrite, MemWrite} = {PCS, RegW, MemW} & {3{CondEx}};
20
21
22     /// Flags Register update
23     always @(posedge CLK)
24     begin
25         if (FlagWrite[1])
26             {N, Z} <= ALUFlags[3:2];
27         if (FlagWrite[0])
28             {C, V} <= ALUFlags[1:0];
29     end
30
31
32     /// Condition Check
33     always @(*)
34     case (Cond)
35         4'b0000:
36             CondEx = Z; // EQ -Equal
37         4'b0001 :
38             CondEx = !Z; // NE - Not equal
39         4'b0010 :
40             CondEx = C; // CS / HS- Carry set / Unsigned higher or same
41         4'b0011 :
42             CondEx = !C; // CC / LO - Carry clear / Unsigned lower
43         4'b0100 :

```


```

44     CondEx = N; // MI - Minus / Negative
45     4'b0101 :
46     CondEx = !N; // PL - Plus / Positive of zero
47     4'b0110 :
48     CondEx = V; // VS - Overflow / Overflow set
49     4'b0111 :
50     CondEx = !V; // VC - No overflow / Overflow clear
51     4'b1000 :
52     CondEx = !V & C; // HI - Unsigned lower or same
53     4'b1001 :
54     CondEx = Z | !C; // LS - Unsigned lower or same
55     4'b1010 :
56     CondEx = !(N ^ V); // GE - Signed greater than or equal
57     4'b1011 :
58     CondEx = N ^ V; // LT - Signed less than
59     4'b1100 :
60     CondEx = !Z & !(N ^ V); // GT - Signed greater than
61     4'b1101 :
62     CondEx = Z | (N ^ V); // LE - Signed less than or equal
63     default:
64     CondEx = 1'b1; // AL - Always / unconditional
65     endcase
66
67     endmodule

```

## Control Unit

File: `ControlUnit.v`

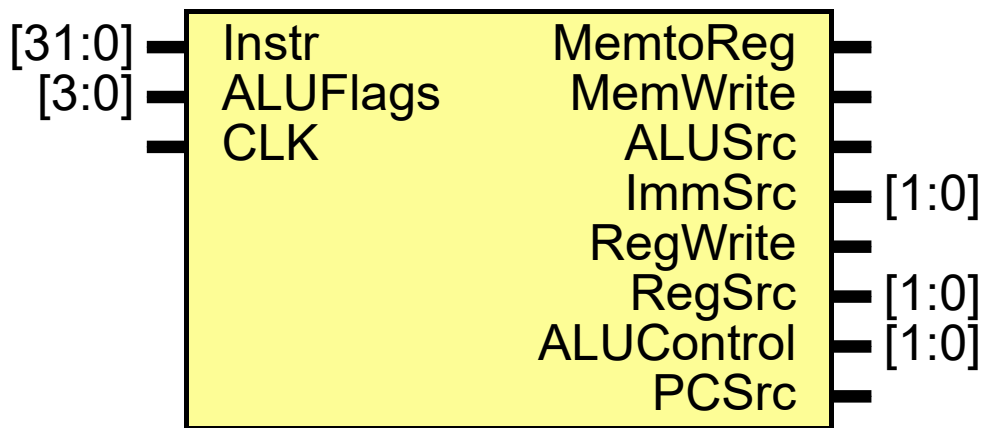

- Ports

Port name	Direction	Type
Instr	input	[31:0]
ALUFlags	input	[3:0]
CLK	input	
MementoReg	output	
MemWrite	output	
ALUSrc	output	
ImmSrc	output	[1:0]
RegWrite	output	
RegSrc	output	[1:0]
ALUControl	output	[1:0]
PCSrc	output	

- Signals

Name	Type
Cond	wire [3:0]
PCS	wire
RegW	wire
MemW	wire
FlagW	wire [1:0]

- Instantiations
- CondLogic1 : CondLogic
- Decoder1 : Decoder
- Verilog Implementation

```

1  `include "Decoder.v"
2  `include "CondLogic.v"
3
4  module ControlUnit(
5      input [31:0] Instr,
6      input [3:0] ALUFlags,
7      input CLK,
8
9      output MementoReg,
10     output MemWrite,
11     output ALUSrc,
12     output [1:0] ImmSrc,
13     output RegWrite,
14     output [1:0] RegSrc,

```


```

15     output [1:0] ALUControl,
16     output PCSrc);
17
18     wire [3:0] Cond = Instr[31:28];
19     wire PCS, RegW, MemW;
20     wire [1:0] FlagW;
21
22
23     CondLogic CondLogic1(
24         CLK,
25         PCS,
26         RegW,
27         MemW,
28         FlagW,
29         Cond,
30         ALUFlags,
31
32         PCSrc,
33         RegWrite,
34         MemWrite);
35
36     Decoder Decoder1(
37         Instr,
38
39         MemtoReg,
40         MemW,
41         ALUSrc,
42         ImmSrc,
43         RegW,
44         RegSrc,
45         ALUControl,
46         FlagW,
47         PCS);
48
49     endmodule

```

## ALU

File: `ALU.v`

 

- Ports

Port name	Direction	Type
A	input	[31:0]
B	input	[31:0]
ALUControl	input	[1:0]
Result	output	[31:0]
ALUFlags	output	[3:0]

- Signals

Name	Type	Description
AddIn	reg [31:0]	FullAdder32
Sum	wire [31:0]	
Cout	wire	
Cin	wire	
N	reg	
Z	reg	
C	reg	
V	reg	

- Verilog Implementation

```

1  module ALU(
2      input [31:0] A,
3      input [31:0] B,
4      input [1:0] ALUControl,
5
6      output reg [31:0] Result,
7      output [3:0] ALUFlags
8  );
9
10
11  //! FullAdder32
12  reg [31:0] AddIn;
13  wire [31:0] Sum;
14  wire Cout;
15  wire Cin = ALUControl[0];
16  FullAdder32 fulladder(A, AddIn, Cin, Sum, Cout);
17
18  //! Result
19  always @(*)
20      begin: Result_Define
21          if (Cin)
22              AddIn = ~B;
23          else
24              AddIn = B;

```

```

25
26     case (ALUControl)
27         2'b11:
28             Result = A | B;
29         2'b10:
30             Result = A & B;
31         default:
32             Result = Sum;
33     endcase
34 end
35
36 reg N, Z, C, V;
37 //! Flags
38 always @(*)
39     begin: Flags_Set
40         Z = ~(|Result);
41         N = Result[31];
42         C = ~ALUControl[1] & Cout;
43         V = ~ALUControl[1] & (A[31] ^ Sum[31]) & ~(A[31] ^ B[31] ^ Cin);
44     end
45
46     assign ALUFlags = {N, Z, C, V};
47
48 endmodule
49
50 module FullAdder1(
51     input A,
52     input B,
53     input Cin,
54     output Sum,
55     output Cout);
56
57     assign Sum = A ^ B ^ Cin;
58     assign Cout = (A & B) | (A ^ B) & Cin;
59 endmodule
60
61 module FullAdder32 (
62     input [31:0] A,
63     input [31:0] B,
64     input Cin,
65     output [31:0] Sum,
66     output Cout);
67
68     wire [31:0] Cout_tmp;
69
70     FullAdder1 fulladder0(
71         A[0],
72         B[0],
73         Cin,
74         Sum[0],
75         Cout_tmp[0]);
76
77     genvar i;
78     generate
79         for(i = 1; i <= 31; i = i + 1)
80             begin: adder_gen
81                 FullAdder1 fulladder(
82                     .A(A[i]),

```


```

83             .B(B[i]),
84             .Cin(Cout_tmp[i - 1]),
85             .Sum(Sum[i]),
86             .Cout(Cout_tmp[i]));
87     end
88 endgenerate
89
90 assign Cout = Cout_tmp[31];
91 endmodule

```

## Extend

File: Extend.v

 

- Ports

Port name	Direction	Type
InstrImm	input	[23:0]
ImmSrc	input	[1:0]
ExtImm	output	[31:0]

## Single Cycle Processor

The previously implemented modules are connected to form the single cycle processor.

```

1  module ARMcore_top(
2      input wire CLK,
3      input wire Reset
4  );
5
6
7      //! ALU instance
8      reg [31:0] SrcA, SrcB;
9      wire [1:0] ALUControl;
10
11     wire [31:0] ALUResult;
12     wire [3:0] ALUFlags;
13
14     ALU alu(
15         .A(SrcA),
16         .B(SrcB),
17         .ALUControl(ALUControl),
18
19         .Result(ALUResult),
20         .ALUFlags(ALUFlags)
21     );
22
23

```

```

24    ///! ControlUnit instance
25    wire [31:0] Instr;
26
27    wire MemtoReg, MemWrite, ALUSrc;
28    wire [1:0] ImmSrc;
29    wire RegWrite;
30    wire [1:0] RegSrc;
31    wire PCSrc;
32
33    ControlUnit controlUnit(
34        .Instr(Instr),
35        .ALUFlags(ALUFlags),
36        .CLK(CLK),
37
38        .MemtoReg(MemtoReg),
39        .MemWrite(MemWrite),
40        .ALUSrc(ALUSrc),
41        .ImmSrc(ImmSrc),
42        .RegWrite(RegWrite),
43        .RegSrc(RegSrc),
44        .ALUControl(ALUControl),
45        .PCSrc(PCSrc)
46    );
47
48
49    ///! Extend instance
50    wire [23:0] InstrImm = Instr[23:0];
51    wire [31:0] ExtImm;
52
53    Extend extend(
54        .InstrImm(InstrImm),
55        .ImmSrc(ImmSrc),
56
57        .ExtImm(ExtImm)
58    );
59
60
61    ///! ProgramCounter instance
62    wire [31:0] PC;
63    wire [31:0] PCPlus4;
64    reg [31:0] Result;
65
66    ProgramCounter programCounter(
67        .CLK(CLK),
68        .Reset(Reset),
69        .PCSrc(PCSrc),
70        .Result(Result),
71
72        .PC(PC),
73        .PC_Plus_4(PCPlus4)
74    );
75
76
77    ///! RegisterFile instance
78    reg [3:0] A1, A2;
79    wire [3:0] A3 = Instr[15:12];
80    wire [31:0] PCPlus8 = PCPlus4 + 4;
81    wire [31:0] RD1, RD2;

```



```

82
83     RegisterFile registerFile(
84         .CLK(CLK),
85         .WE3(RegWrite),
86         .A1(A1),
87         .A2(A2),
88         .A3(A3),
89         .WD3(Result),
90         .R15(PCPlus8),
91
92         .RD1(RD1),
93         .RD2(RD2)
94     );
95
96     always @(*)
97     begin
98         if (RegSrc[0])
99             A1 = 4'b1111;
100        else
101            A1 = Instr[19:16];
102
103        if (RegSrc[1])
104            A2 = Instr[15:12];
105        else
106            A2 = Instr[3:0];
107
108        if (ALUSrc)
109            SrcB = ExtImm;
110        else
111            SrcB = RD2;
112
113        SrcA = RD1;
114    end
115
116    /// InstrMem instance
117    InstrMem instrMem(
118        .PC(PC),
119        .Instr(Instr)
120    );
121
122
123    /// DataMem instance
124    wire [31:0] RD;
125    DataMem dataMem(
126        .CLK(CLK),
127        .Address(ALUResult),
128        .WE(MemWrite),
129        .WD(RD2),
130
131        .ReadData(RD)
132    );
133
134    always @(*)
135    if (MemtoReg)
136        Result = RD;
137    else
138        Result = ALUResult;
139

```

```

140
141     endmodule

```

## Testbench

The basic idea for the testbench is to make each of the instruction depend on the previous result, such that, if the final result is correct, it is relatively confident to conclude that the processor performs as expected for each of the instructions.

After the testbench is composed, it is then compiled using **Keil uVision5**. The corresponding instructions and data are initialized in **DataMem.v** and **InstrMem.v**. Simulation is then performed with Vivado and ModelSim.

### Testbench for Memory Operations

We first test for the memory operations, namely **LDR** and **STR** instructions. Since **MOV** instruction is not available in our implementation, we use **AND** operation to initialize **R0** with **0**, which is then used as the base address for loading data from **DATA\_MEM**. The loaded values in the registers can be utilized in subsequent tests.

```


1  ; Test for LDR
2  AND R0, R0, #0      ; initialize R0 as 0, R0 = 0x00000000
3  LDR R1, [R0, #1]    ; R1 = DATA_MEM[1], 0x0000_000F
4  LDR R2, [R0, #2]    ; R2 = DATA_MEM[2], 0x0000_00F0
5  LDR R3, [R0, #3]    ; R3 = DATA_MEM[3], 0x0000_0F00
6  LDR R4, [R0, #4]    ; R4 = DATA_MEM[4], 0x0000_F000
7  LDR R5, [R0, #5]    ; R5 = DATA_MEM[5], 0x0F0F_0F0F
8  LDR R6, [R0, #6]    ; R6 = DATA_MEM[6], 0xF0F0_F0F0

```

The corresponding HEX value is

1	0x00000000	E2000000	AND	R0, R0, #0x00000000
2	0x00000004	E5901001	LDR	R1, [R0, #0x0001]
3	0x00000008	E5902002	LDR	R2, [R0, #0x0002]
4	0x0000000C	E5903003	LDR	R3, [R0, #0x0003]
5	0x00000010	E5904004	LDR	R4, [R0, #0x0004]
6	0x00000014	E5905005	LDR	R5, [R0, #0x0005]
7	0x00000018	E5906006	LDR	R6, [R0, #0x0006]

The simulation waveform is shown below.

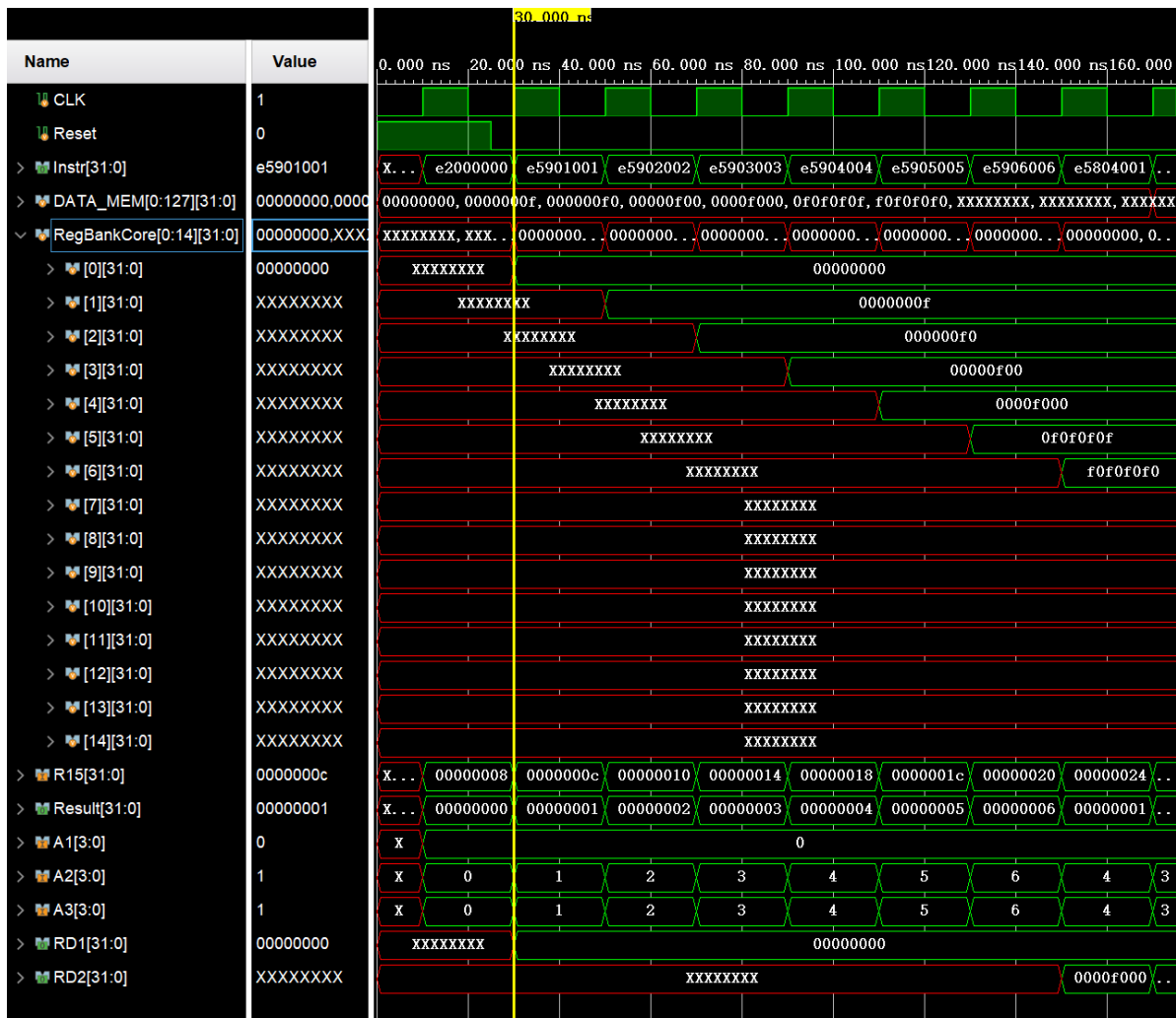

According to the waveform form from 30ns to 160ns, signal **RegBankCore** clearly shows that the expected data are initialized and loaded into **R0** through **R6**.

Afterwards, we write the data from the register file back into the data memory in reverse order.

```

1  ; Test for STR
2  STR R4, [R0, #1]    ; DATA_MEM[1] = R4, 0x0000_F000
3  STR R3, [R0, #2]    ; DATA_MEM[2] = R3, 0x0000_0F00
4  STR R2, [R0, #3]    ; DATA_MEM[3] = R2, 0x0000_00F0
5  STR R1, [R0, #4]    ; DATA_MEM[4] = R1, 0x0000_000F

```


The corresponding HEX value is

```

1  0x0000001C E5804001 STR R4, [R0, #0x0001]
2  0x00000020 E5803002 STR R3, [R0, #0x0002]
3  0x00000024 E5802003 STR R2, [R0, #0x0003]
4  0x00000028 E5801004 STR R1, [R0, #0x0004]

```

The simulation waveform is shown below.

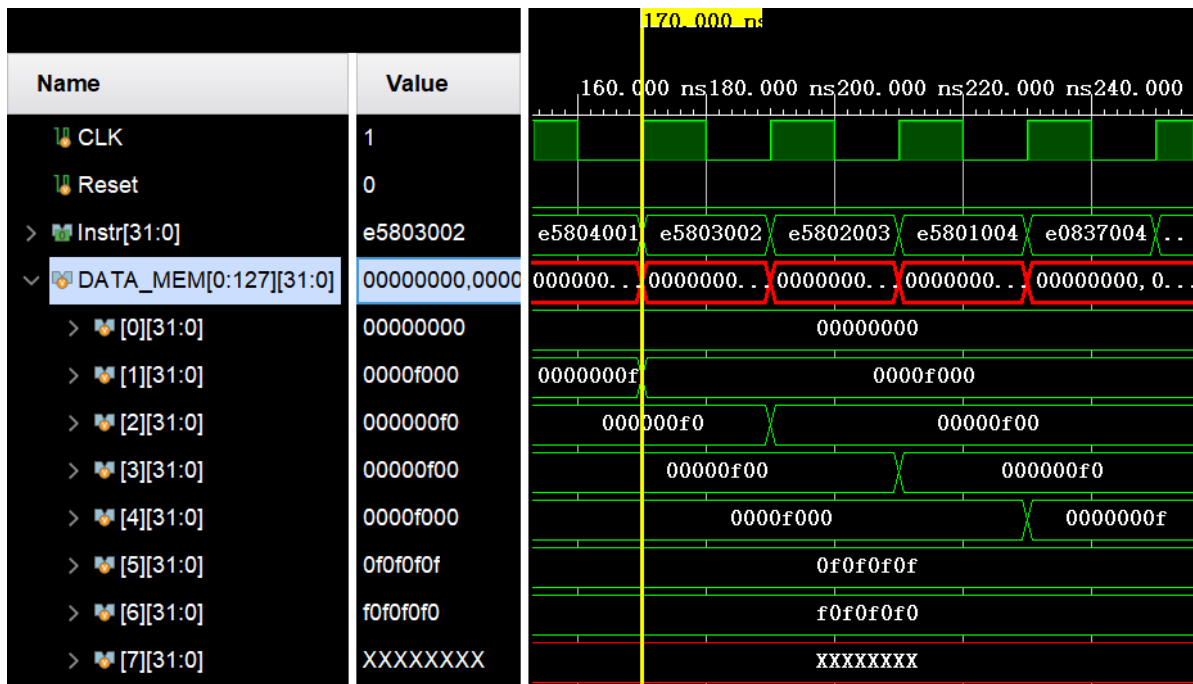

According to the waveform form of signal `DATA_MEM` from 170ns to 240ns, the data in the data memory are modified as expected.

Thus, we may conclude that the CPU performs memory operations normally.

## Testbench for Data-Path Operations

The testbench for Data-Path operations, namely the `ADD`, `SUB`, `AND` and `ORR` instructions, consists of a sequence of instructions, each depends on the result from its preceding instruction. Both immediate number and register as `Src2` are included.

```


1  ; Test for DP instructions
2  ADD R7, R3, R4      ; R7 = 0x0000_FF00
3  ADD R7, R7, #0xFF   ; R7 = 0x0000_FFFF
4  SUB R7, R7, R2      ; R7 = 0x0000_FF0F
5  SUB R7, R7, #0xE    ; R7 = 0x0000_FF01
6  AND R7, R7, R5      ; R7 = 0x0000_0F01
7  AND R7, R7, #0xFF   ; R7 = 0x0000_0001
8  ORR R7, R7, R6      ; R7 = 0xF0F0_F0F1
9  ORR R7, R7, #0      ; R7 = 0xF0F0_F0F1

```

The corresponding HEX value is

1	0x0000002C	E0837004	ADD	R7, R3, R4
2	0x00000030	E28770FF	ADD	R7, R7, #0x000000FF
3	0x00000034	E0477002	SUB	R7, R7, R2
4	0x00000038	E247700E	SUB	R7, R7, #0x0000000E
5	0x0000003C	E0077005	AND	R7, R7, R5
6	0x00000040	E20770FF	AND	R7, R7, #0x000000FF
7	0x00000044	E1877006	ORR	R7, R7, R6
8	0x00000048	E3877000	ORR	R7, R7, #0x00000000
9	0x0000004C	E3818000	ORR	R8, R1, #0x00000000

The simulation waveform is shown below.

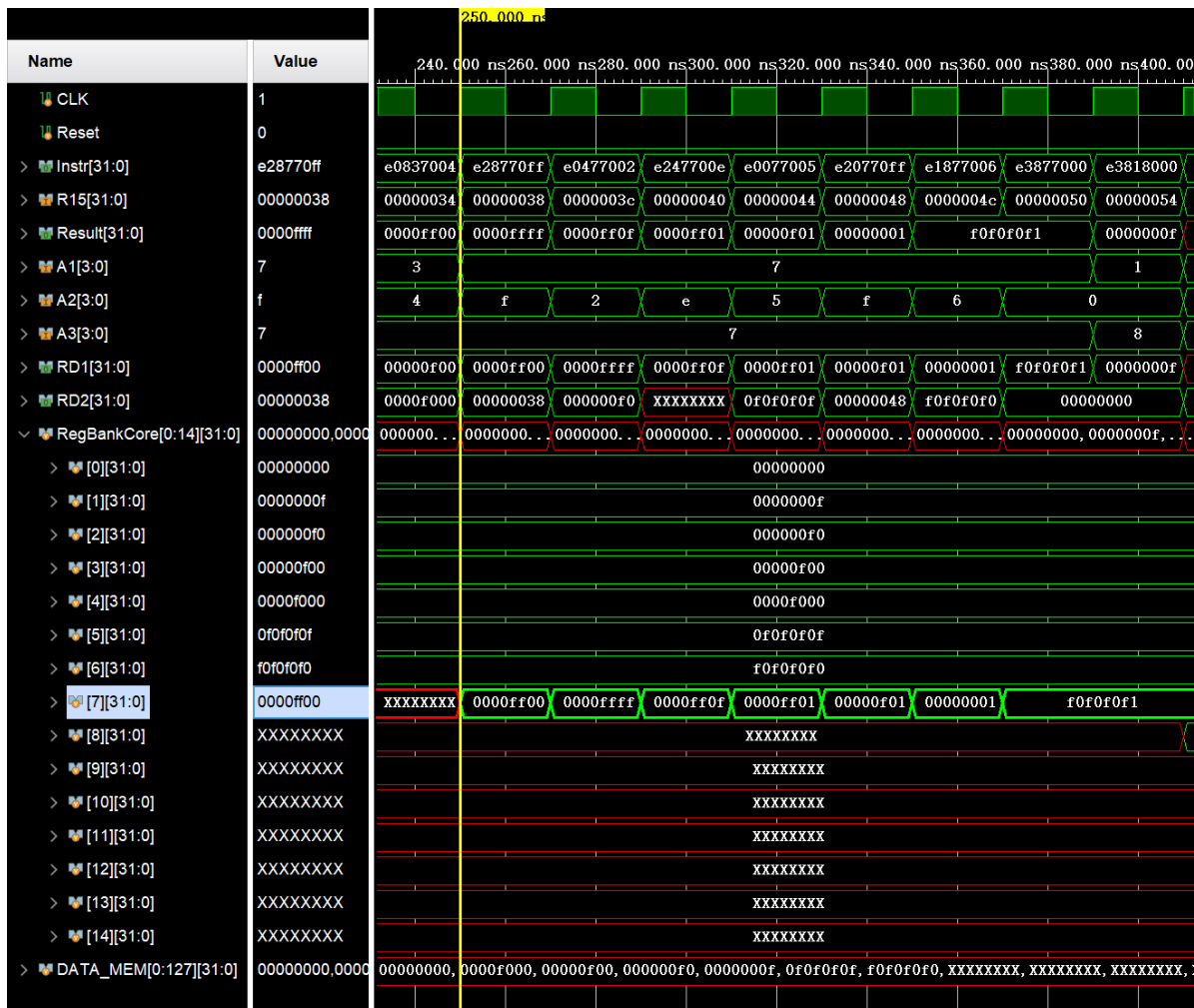

According to the waveform form of signal **RegBankCore** and **Result[31:0]** from 240ns to 420ns, the final result, as well as each intermediate result of the DP instructions are expected.

## Testbench for Branch Instruction

The testbench for branch instruction consists of a loop for increment of one register and decrement of another.

```

1      ; Test for Branch instruction
2      ORR R8, R1, #0    ; R8 = R1 = 0xF
3      AND R9, R9, #0    ; R9 = 0x0
4      LOOP
5      SUBS R8, R8, #1    ; Update R8 and set flags, R8--
6      ADD R9, R9, #1    ; Update R9, R9++
7      BNE LOOP          ; LOOP until R8 = 0

```

After the loop exits, **R8** should decrease to **0**, while **R9** takes the original value of **R8** before the loop.


The corresponding HEX value is

```

1      0x00000058 E2899000 AND      R9, R9, #0x00000000
2      0x00000054 E2588001 SUBS     R8, R8, #0x00000001
3      0x00000058 E2899001 ADD      R9, R9, #0x00000001
4      0x0000005C 1AFFFFFC BNE      0x00000054

```

The simulation waveform is shown below.

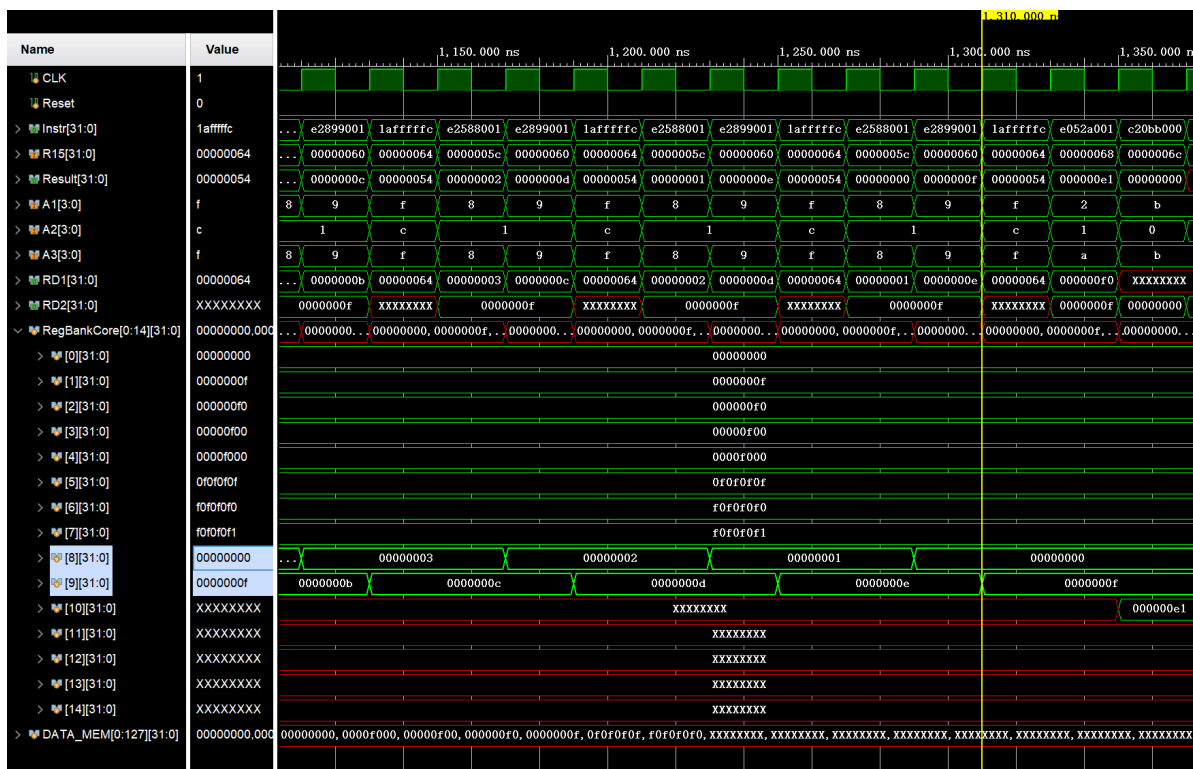

According to the waveform of signal **RegBankCore** , the loop is executed and exited correctly.

## Testbench for Flags and Condition Logic

Since the amount of possible conditions for instructions is too large, we here only consider the **HI** , **LS** , **GT** , and **LE** conditions and thus have covered all 4 of the **N** , **Z** , **C** , and **V** ALU flags.

cond	Mnemonic	Name	CondEx
1000	HI	Unsigned higher	!Z & C
1001	LS	Unsigned lower or same	Z   !C
1100	GT	Signed greater than	!Z & !(N ^ V)
1101	LE	Signed less than or equal	Z   (N ^ V)

The assembly instructions is shown in the code blocks below.

```

1  ; Test for flags and condition
2  SUBS R10, R2, R1
3  ANDGT R11, R0, #0      ; GT should be TRUE, R11 = 0
4  ADDLE R11, R11, #0xF    ; LE should be FALSE, R11 = 0
5  ANDHI R12, R0, #0      ; HI should be TRUE, R12 = 0
6  ADDLS R12, R12, #0xF    ; LS should be FALSE, R12 = 0


```

Ideally, since **R2** is greater than **R1** in both signed and unsigned arithmetics, the **SUBS** instruction would set the ALU flags as **NZCV = 0000** , and thus **GT** and **HI** hold true, **LE** and **LS** should be false.

The corresponding HEX value is

1	0x00000060	E052A001	SUBS	R10, R2, R1
2	0x00000064	C200B000	ANDGT	R11, R0, #0x00000000
3	0x00000068	D28BB00F	ADDLE	R11, R11, #0x0000000F
4	0x0000006C	8200C000	ANDHI	R12, R0, #0x00000000
5	0x00000070	928CC00F	ADDLS	R12, R12, #0x0000000F

The simulation waveform is shown below.

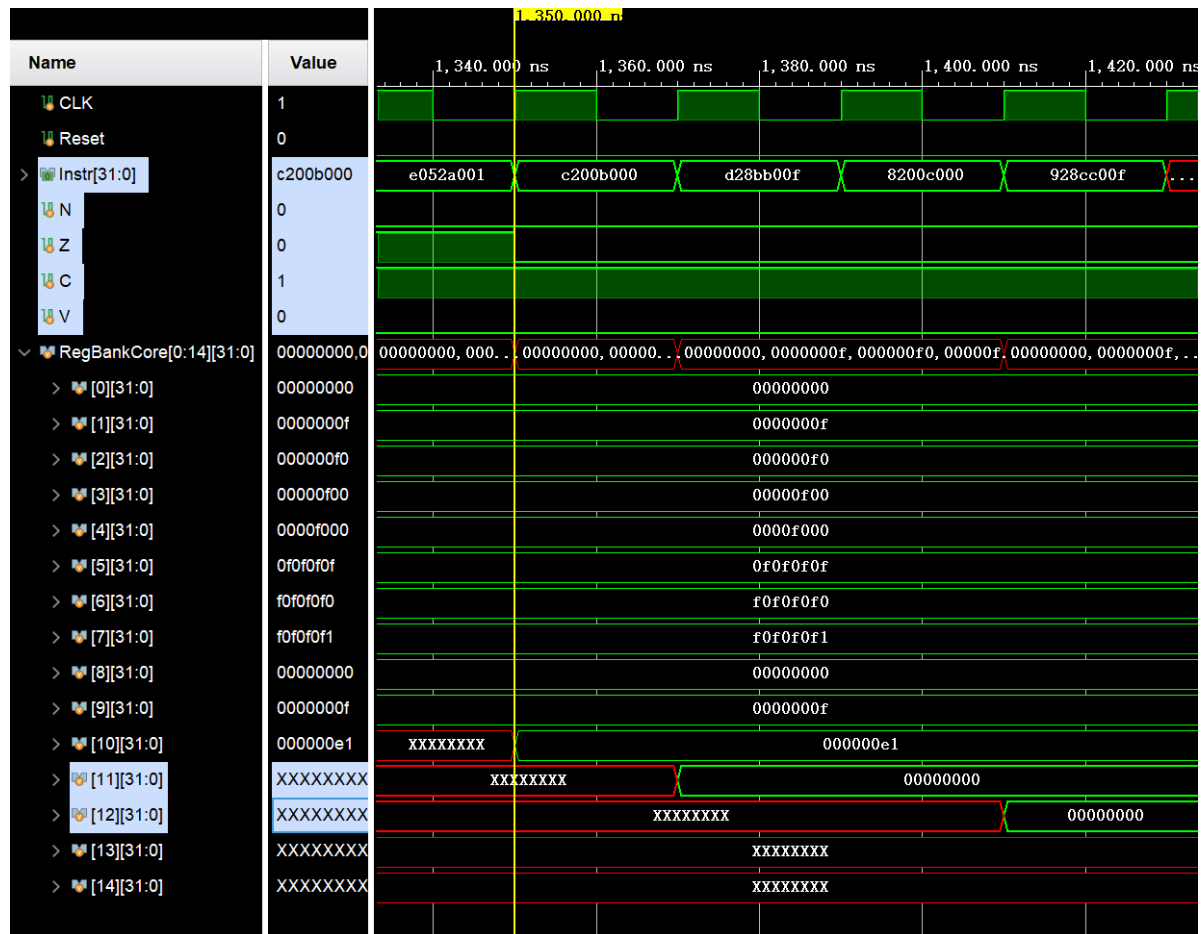

According to the waveform, the values stored in the Flag registers are correct, and the conditioned instructions are executed as expected.

## Conclusion

Since the testbench has covered a large percentage of the categories of instructions, we can conclude that this implementation of single-cycle processor functions normally, though some minor bugs might take place in certain extreme cases.